

Worksheet 7

To accompany Chapter 3.4 Transfer Functions

Colophon

This worksheet can be downloaded as a [PDF file](#). We will step through this worksheet in class.

An annotatable copy of the notes for this presentation will be distributed before the second class meeting as **Worksheet 7** in the **Week 3: Classroom Activities** section of the Canvas site. I will also distribute a copy to your personal **Worksheets** section of the **OneNote Class Notebook** so that you can add your own notes using OneNote.

You are expected to have at least watched the video presentation of [Chapter 3.4](#) of the [notes](#) before coming to class. If you haven't watch it afterwards!

After class, the lecture recording and the annotated version of the worksheets will be made available through Canvas.

Agenda

- Transfer Functions
- A Couple of Examples
- Circuit Analysis Using MATLAB LTI Transfer Function Block
- Circuit Simulation Using Simulink Transfer Function Block


```
In [1]: % Matlab setup
clear all
cd ../matlab
pwd
imatlabs_export_fig('print-svg') % Static svg figures.
format compact

ans =
/Users/eechris/code/src/github.com/cpjobling/eg-247-textbook/laplace_transform/matlab'
```

Transfer Functions for Circuits

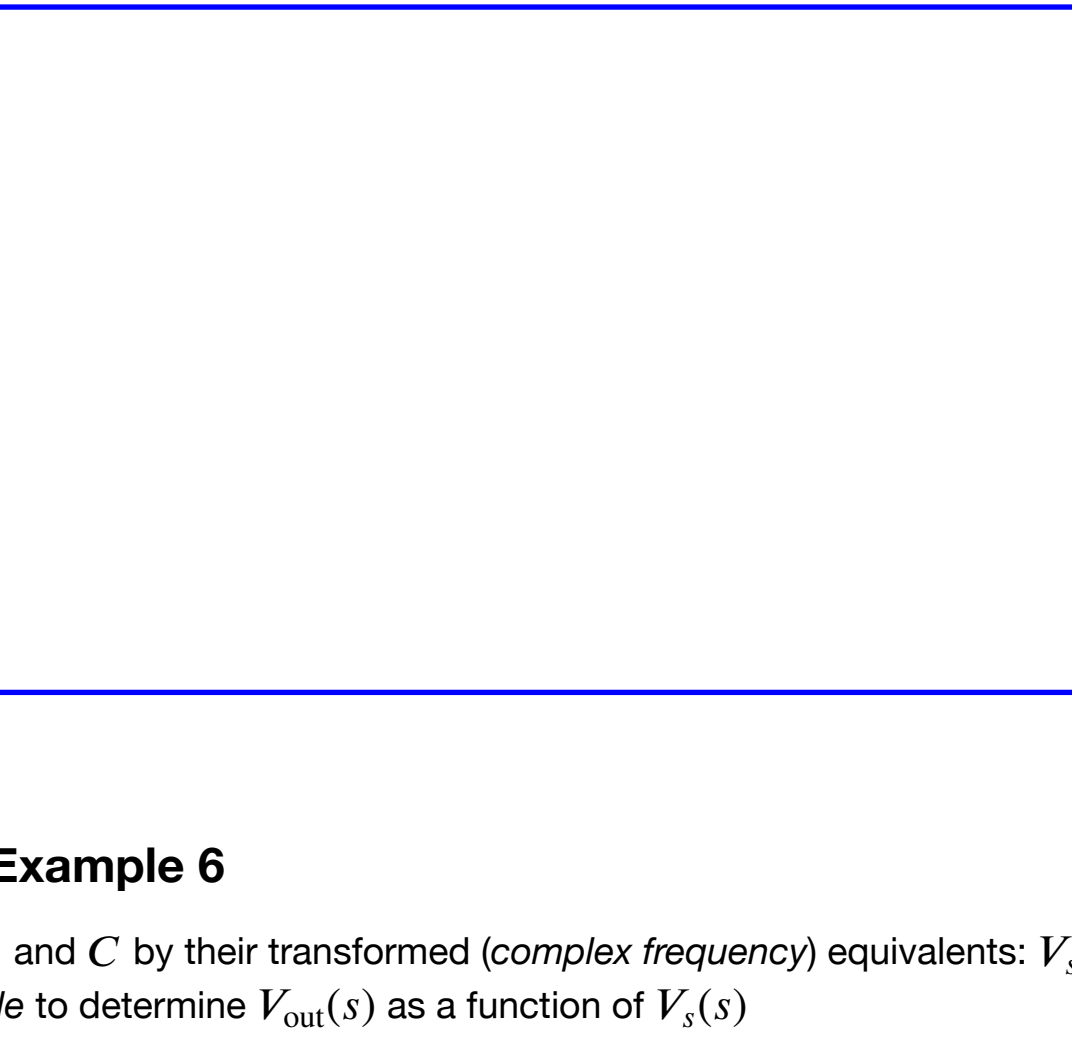Example 6

Derive an expression for the transfer function $G(s)$ for the circuit below. In this circuit R_g represents the internal resistance of the applied (voltage) source v_s , and R_L represents the resistance of the load that consists of R_L , L and C .



Sketch of Solution for Example 6

- Replace $v_s(t)$, R_g , R_L , L and C by their transformed (*complex frequency*) equivalents: $V_s(s)$, R_g , R_L , sL and $1/(sC)$
- Use the *Voltage Divider Rule* to determine $V_{out}(s)$ as a function of $V_s(s)$
- Form $G(s)$ by writing down the ratio $V_{out}(s)/V_s(s)$

Worked solution for Example 6

Pencast: [ex6.pdf](#) - open in Adobe Acrobat Reader.

Answer for Example 6



$$G(s) = \frac{V_{out}(s)}{V_s(s)} = \frac{R_L + sL + 1/sC}{R_g + R_L + sL + 1/sC}.$$

Example 7

Compute the transfer function for the op-amp circuit shown below in terms of the circuit constants R_1 , R_2 , R_3 , C_1 and C_2 . Then replace the complex variable s with $j\omega$, and the circuit constants with their numerical values and plot the magnitude

$$|G(j\omega)| = \frac{|V_{out}(j\omega)|}{|V_{in}(j\omega)|}$$

versus radian frequency ω rad/s.

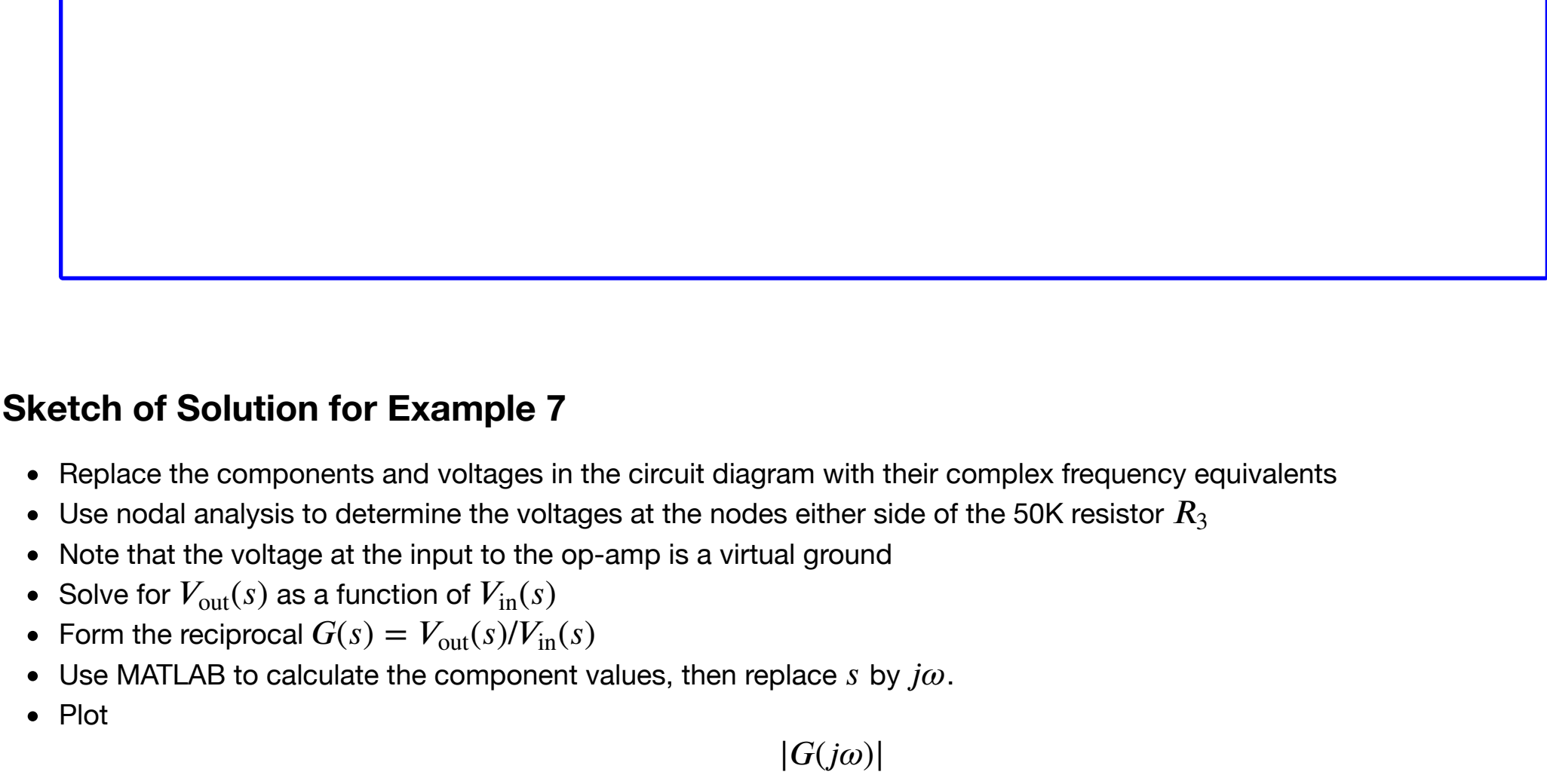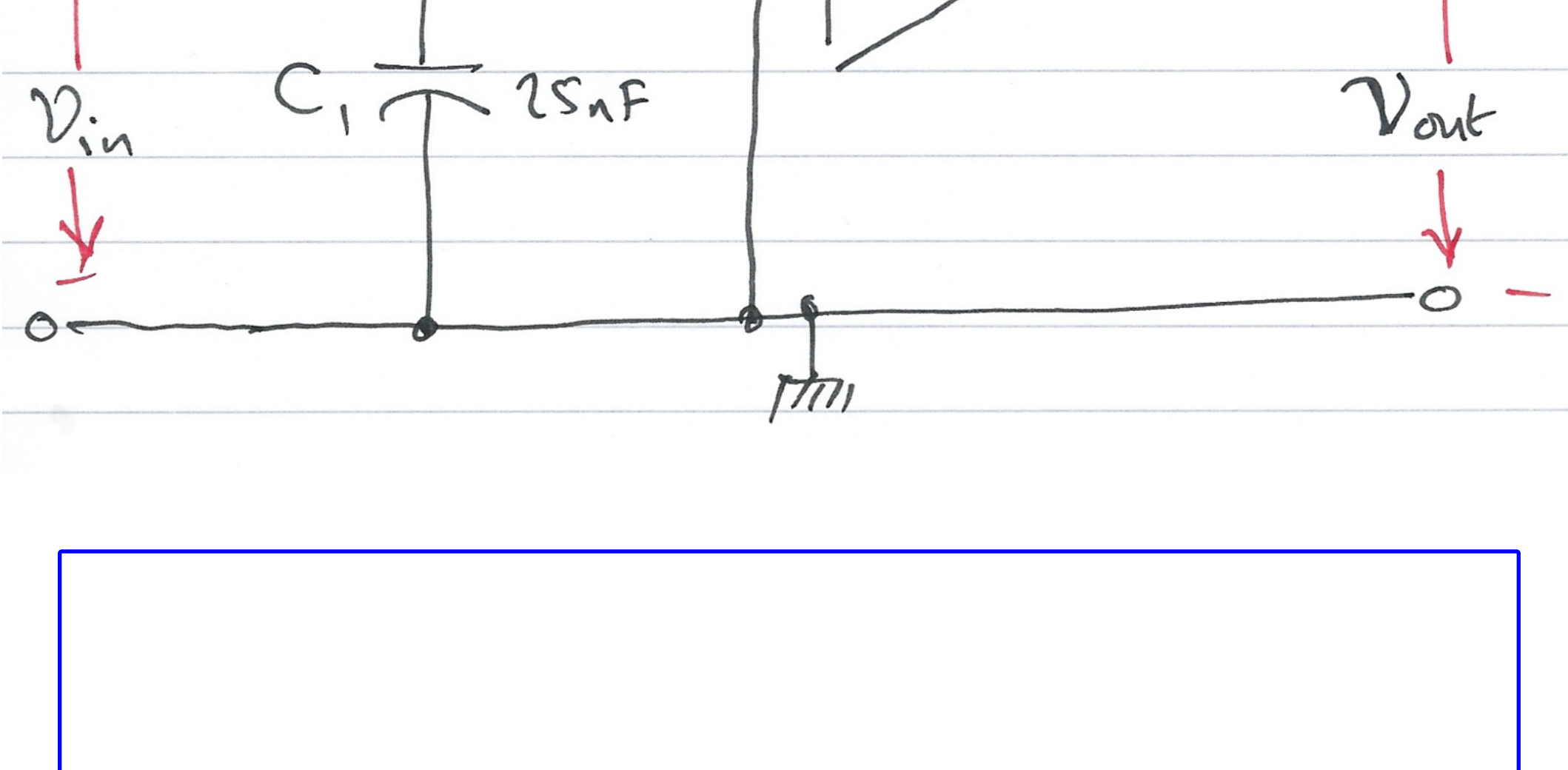

Sketch of Solution for Example 7

- Replace the components and voltages in the circuit diagram with their complex frequency equivalents
- Use nodal analysis to determine the voltages at the nodes either side of the 50K resistor R_3
- Note that the voltage at the input to the op-amp is a virtual ground
- Solve for $V_{out}(s)$ as a function of $V_{in}(s)$
- Form the reciprocal $G(s) = V_{out}(s)/V_{in}(s)$
- Use MATLAB to calculate the component values, then replace s by $j\omega$.
- Plot

$$|G(j\omega)|$$

on log-linear "paper".

Worked solution for Example 7

Pencast: [ex7.pdf](#) - open in Adobe Acrobat Reader.

Answer for Example 7

$$G(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{-1}{R_1 [(1/R_1 + 1/R_2 + 1/R_3 + sC_1)(sC_2R_3) + 1/R_2]}.$$

The Matlab Bit

See attached script: [solution7.m](#).

Week 3: Solution 7

```
In [2]: syms s;

In [3]: R1 = 200*10^3; % 200 kOhm
R2 = 40*10^3; % 40 kOhm
R3 = 50*10^3; % 50 kOhm

C1 = 25*10^(-9); % 25 nF
C2 = 10*10^(-9); % 10 nF

In [4]: den = R1*(1/R1+ 1/R2 + 1/R3 + s*C1)*(s*R3*C2) + 1/R2);
simplify(den)

ans =
100*s*((7555786372591433*s)/302231454903657293676544 + 1/20000) + 5

Result is: 100*s*((7555786372591433*s)/302231454903657293676544 + 1/20000) + 5

Simplify coefficients of s in denominator
```

```
In [7]: format long
denG = sym2poly(ans)

denG =
0.00000025000000000 0.0050000000000000 5.000000000000000
```

```
In [8]: numG = -1;
```

Plot

For convenience, define coefficients a and b :


```
In [9]: a = denG(1);
b = denG(2);
```

```
In [10]: w = 1:10:10000;
```

$$G(j\omega) = \frac{-1}{a\omega^2 - j b\omega + 5}$$

```
In [12]: Gw = -1./((a*w.^2 - j.*b.*w + denG(3)));
```


```
In [13]: semilogx(w, abs(Gw))
xlabel('Radian frequency w (rad/s)')
ylabel('|Vout/Vin|')
title('Magnitude Vout/Vin vs. Radian Frequency')
grid
```

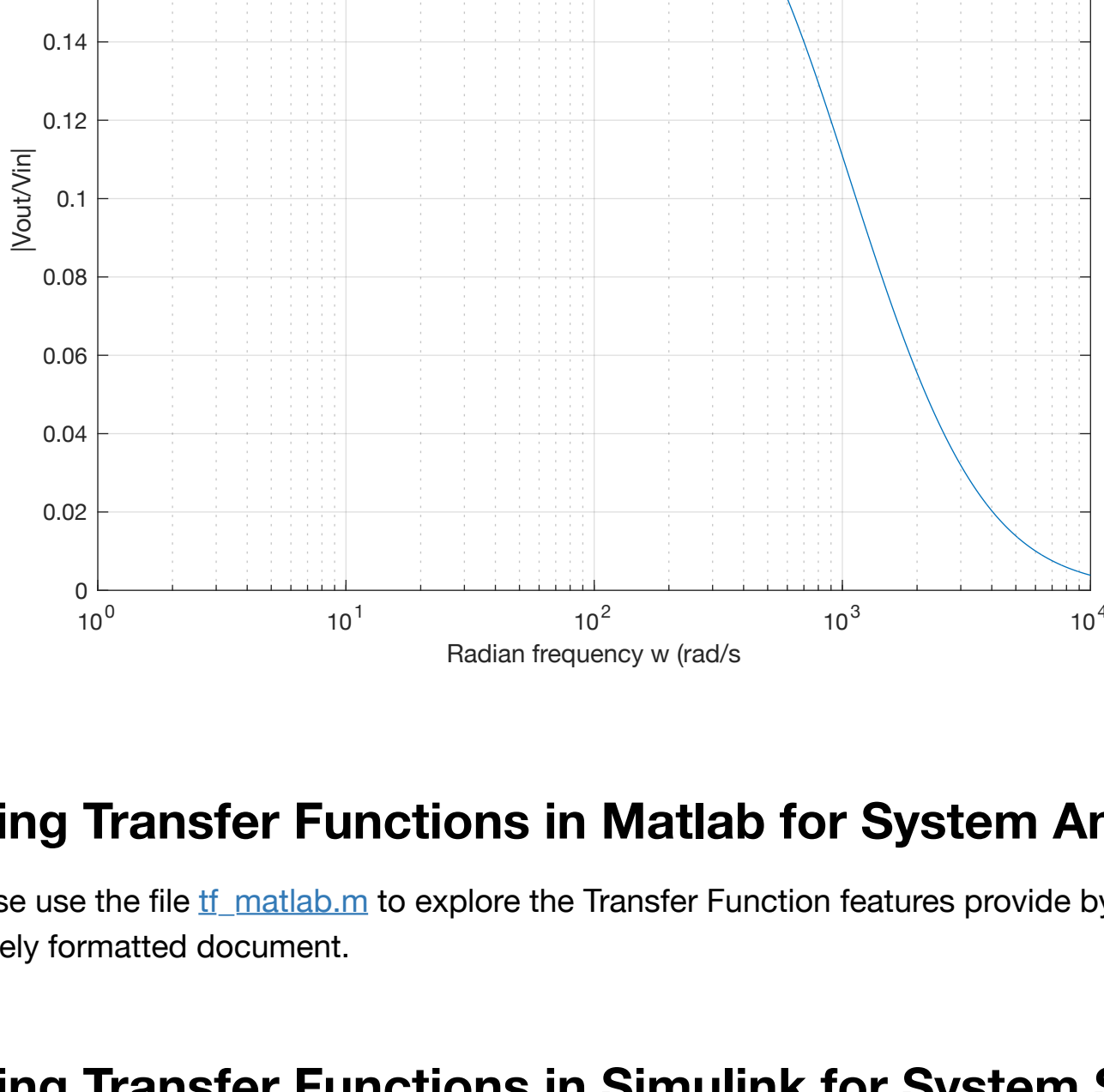

Using Transfer Functions in Matlab for System Analysis

Please use the file [if_matlab.m](#) to explore the Transfer Function features provide by Matlab. Use the *publish* option to generate a nicely formatted document.

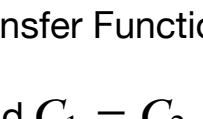Using Transfer Functions in Simulink for System Simulation



The Simulink transfer function (**Transfer Fcn**) block shown above implements a transfer function representing a general input output function

$$G(s) = \frac{N(s)}{D(s)}$$

that it is not specific nor restricted to circuit analysis. It can, however be used in modelling and simulation studies.

Example

Recast Example 7 as a MATLAB problem using the LTI Transfer Function block.

For simplicity use parameters $R_1 = R_2 = R_3 = 1 \Omega$, and $C_1 = C_2 = 1 \text{ F}$.

Calculate the step response using the LTI functions.

Verify the result with Simulink.

The Matlab solution: [example8.m](#)

MATLAB Solution

From a previous analysis the transfer function is:

$$G(s) = \frac{V_{out}}{V_{in}} = \frac{-1}{R_1 [(1/R_1 + 1/R_2 + 1/R_3 + sC_1)(sR_3C_2) + 1/R_2]}$$

so substituting the component values we get:

$$G(s) = \frac{V_{out}}{V_{in}} = \frac{-1}{s^2 + 3s + 1}$$

We can find the step response by letting $v_{in}(t) = u_0(t)$ so that $V_{in}(s) = 1/s$ then

$$V_{out}(s) = \frac{-1}{s^2 + 3s + 1} \cdot \frac{1}{s}$$

We can solve this by partial fraction expansion and inverse Laplace transform as is done in the text book with the help of Matlab's `residue` function.

Here, however we'll use the LTI block that was introduced in the lecture.

Define the circuit as a transfer function

```
In [14]: G = tf([-1],[1 3 1])


G =

-----
s^2 + 3 s + 1

Continuous-time transfer function.
```

step response is then:

```
In [15]: step(G)
```

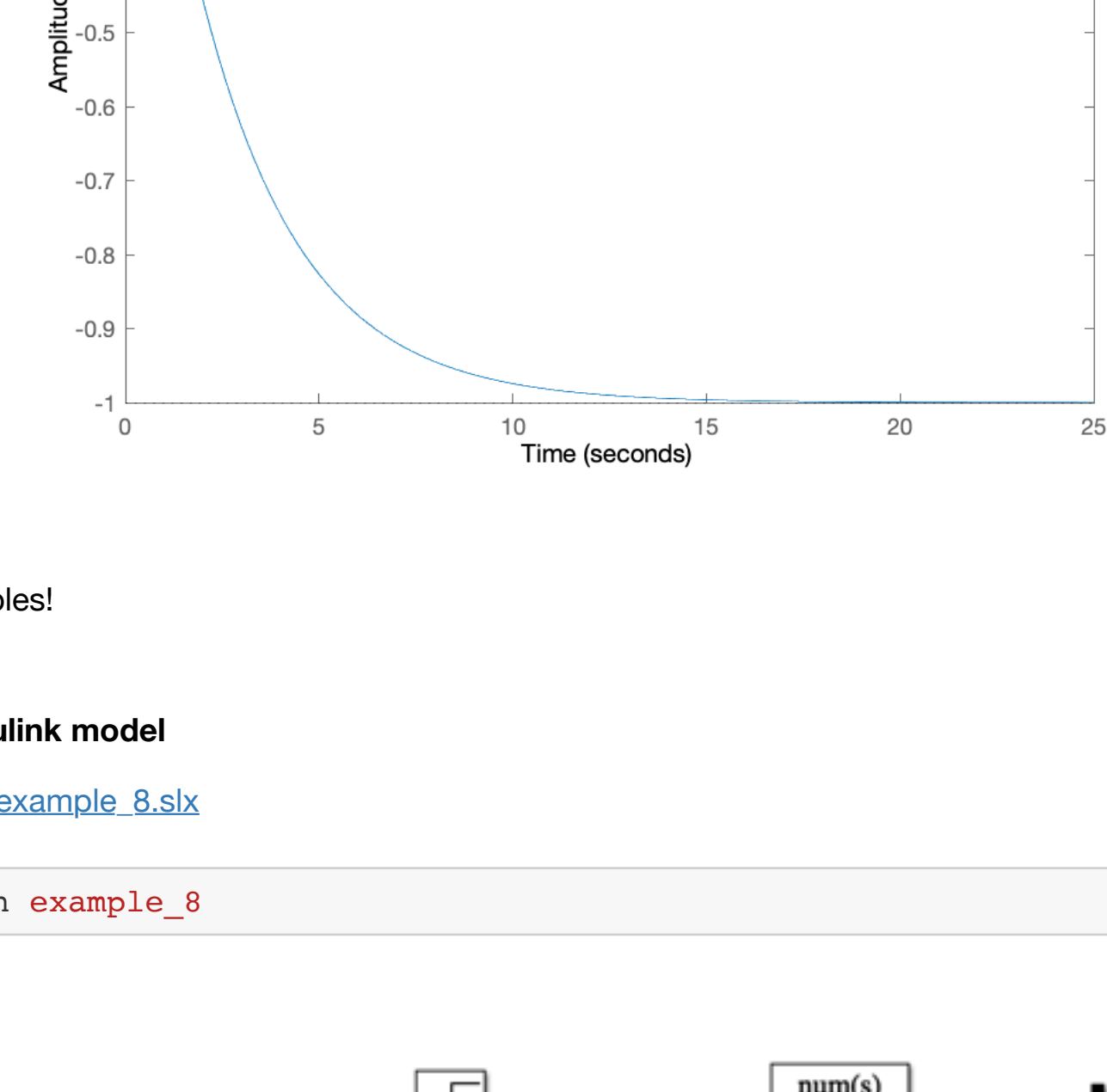


Simples!


Simulink model

See [example 8.slx](#)

```
In [16]: open example_8
```

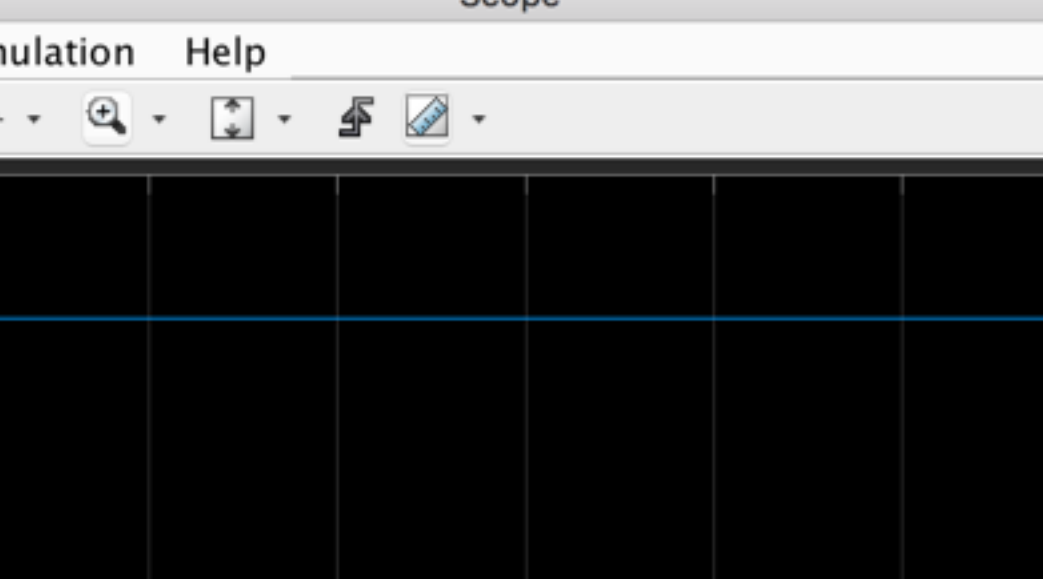


Result

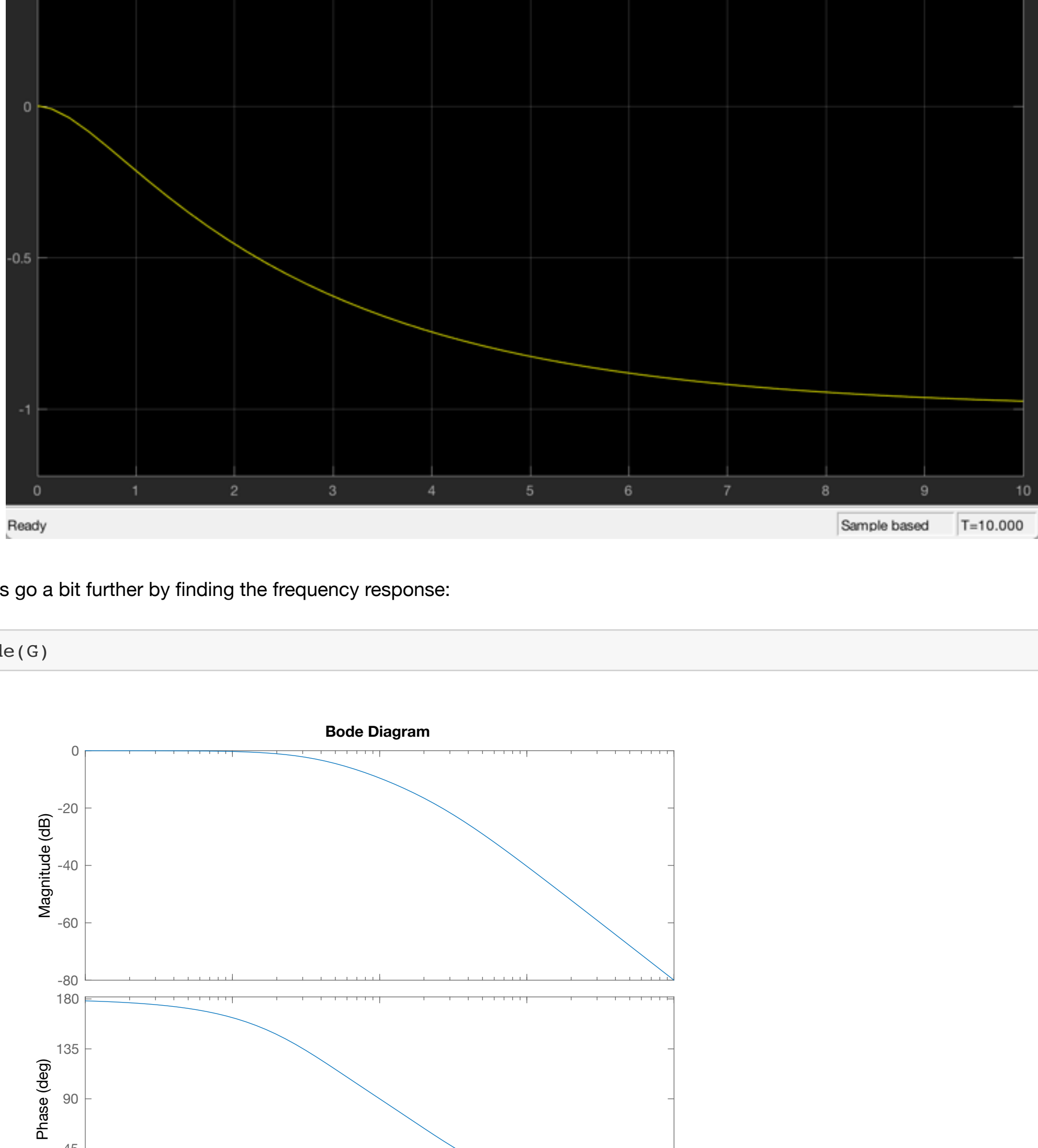

Let's go a bit further by finding the frequency response:

```
In [ ]: bode(G)
```

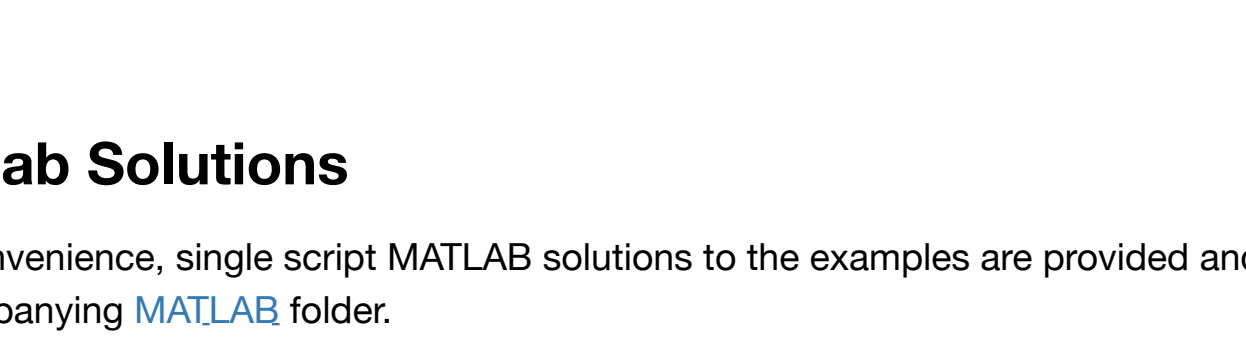

Matlab Solutions

For convenience, single script MATLAB solutions to the examples are provided and can be downloaded from the accompanying [MATLAB](#) folder.

- Solution 7 [[solution7.m](#)]
- Example 8 [[example8.m](#)]
- Simulink model [[example_8.slx](#)]

```
In [ ]: cd ../matlab
ls
open solution7
```