

# Worksheet 7

## Contents

- [To accompany Unit 3.4 Transfer Functions](#)
- [Colophon](#)
- [Agenda](#)
- [Transfer Functions for Circuits](#)
- [Using Transfer Functions in Matlab for System Analysis](#)
- [Using Transfer Functions in Simulink for System Simulation](#)
- [Matlab Solutions](#)

## To accompany Unit 3.4 Transfer Functions

## Colophon

This worksheet can be downloaded as a [PDF file](#). We will step through this worksheet in class.

An annotatable copy of the notes for this presentation will be distributed before the second class meeting as **Worksheet 7** in the **Week 3: Classroom Activities** section of the Canvas site. I will also distribute a copy to your personal **Worksheets** section of the **OneNote Class Notebook** so that you can add your own notes using OneNote.

You are expected to have at least watched the video presentation of [Chapter 3.4](#) of the [notes](#) before coming to class. If you haven't watch it afterwards!

After class, the lecture recording and the annotated version of the worksheets will be made available through Canvas.

## Agenda


- Transfer Functions
- A Couple of Examples
- Circuit Analysis Using MATLAB LTI Transfer Function Block
- Circuit Simulation Using Simulink Transfer Function Block

```
% Matlab setup
clear all
cd ../matlab
pwd
format compact
```

## Transfer Functions for Circuits
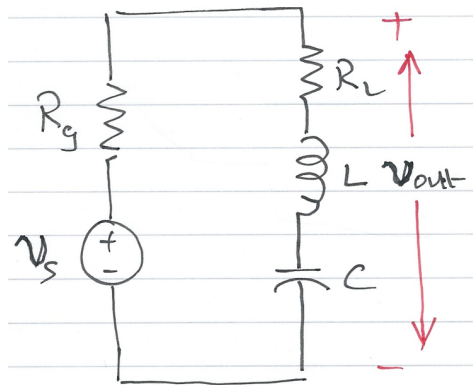
### Example 6

Derive an expression for the transfer function  $G(s)$  for the circuit below. In this circuit  $R_g$  represents the internal resistance of the applied (voltage) source  $v_s$ , and  $R_L$  represents the resistance of the load that consists of  $R_L$ ,  $L$  and  $C$ .



### Sketch of Solution for Example 6

- Replace  $v_s(t)$ ,  $R_g$ ,  $R_L$ ,  $L$  and  $C$  by their transformed (complex frequency) equivalents:  $V_s(s)$ ,  $R_g$ ,  $R_L$ ,  $sL$  and  $1/(sC)$
- Use the *Voltage Divider Rule* to determine  $V_{out}(s)$  as a function of  $V_s(s)$
- Form  $G(s)$  by writing down the ratio  $V_{out}(s)/V_s(s)$

### Worked solution for Example 6

Pencast: [ex6.pdf](#) - open in Adobe Acrobat Reader.

### Answer for Example 6


$$G(s) = \frac{V_{\text{out}}(s)}{V_s(s)} = \frac{R_L + sL + 1/sC}{R_g + R_L + sL + 1/sC}.$$

## Example 7

Compute the transfer function for the op-amp circuit shown below in terms of the circuit constants  $R_1$ ,  $R_2$ ,  $R_3$ ,  $C_1$  and  $C_2$ . Then replace the complex variable  $s$  with  $j\omega$ , and the circuit constants with their numerical values and plot the magnitude

$$|G(j\omega)| = \frac{|V_{\text{out}}(j\omega)|}{|V_{\text{in}}(j\omega)|}$$

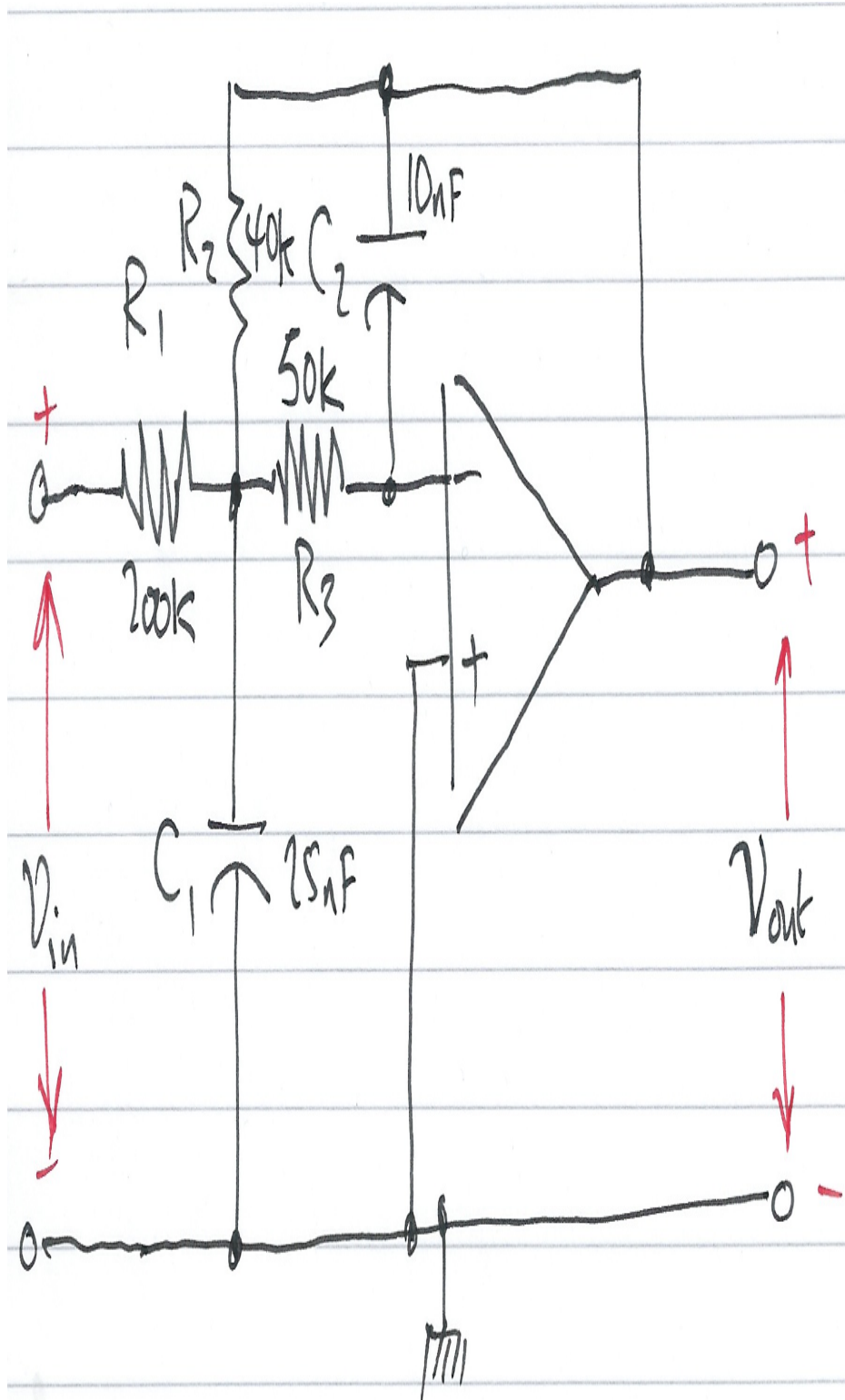versus radian frequency  $\omega$  rad/s.



## Sketch of Solution for Example 7

- Replace the components and voltages in the circuit diagram with their complex frequency equivalents
- Use nodal analysis to determine the voltages at the nodes either side of the 50K resistor  $R_3$
- Note that the voltage at the input to the op-amp is a virtual ground
- Solve for  $V_{\text{out}}(s)$  as a function of  $V_{\text{in}}(s)$
- Form the reciprocal  $G(s) = V_{\text{out}}(s)/V_{\text{in}}(s)$
- Use MATLAB to calculate the component values, then replace  $s$  by  $j\omega$ .
- Plot  $|G(j\omega)|$  on log-linear "paper".

## Worked solution for Example 7

Pencast: [ex7.pdf](#) - open in Adobe Acrobat Reader.

## Answer for Example 7

$$G(s) = \frac{V_{\text{out}}(s)}{V_{\text{in}}(s)} = \frac{-1}{R_1 \left( (1/R_1 + 1/R_2 + 1/R_3 + sC_1)(sC_2R_3) + 1/R_2 \right)}.$$

## The Matlab Bit

See attached script: [solution7.m](#).

## Week 3: Solution 7

```
syms s;
```

```
R1 = 200*10^3; % 200 kOhm
R2 = 40*10^3; % 40 kOhm
R3 = 50*10^3; % 50 kOhm

C1 = 25*10^(-9); % 25 nF
C2 = 10*10^(-9); % 10 nF
```

```
den = R1*((1/R1+ 1/R2 + 1/R3 + s*C1)*(s*R3*C2) + 1/R2);
simplify(den)
```

Result is:  $100*s*((7555786372591433*s)/302231454903657293676544 + 1/20000) + 5$

Simplify coefficients of  $s$  in denominator

```
format long
denG = sym2poly(ans)
```

```
numG = -1;
```

Plot

For convenience, define coefficients  $a$  and  $b$ :

```
a = denG(1);
b = denG(2);
```

```
w = 1:10:10000;
```

$$G(j\omega) = \frac{-1}{a\omega^2 - jb\omega + 5}$$


```
Gw = -1./(a*w.^2 - j.*b.*w + denG(3));
```

```
semilogx(w, abs(Gw))
xlabel('Radian frequency w (rad/s)')
ylabel('|Vout/Vin|')
title('Magnitude Vout/Vin vs. Radian Frequency')
grid
```

## Using Transfer Functions in Matlab for System Analysis

Please use the file [tf\\_matlab.m](#) to explore the Transfer Function features provide by Matlab. Use the *publish* option to generate a nicely formatted document.
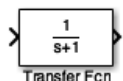
## Using Transfer Functions in Simulink for System Simulation



The Simulink transfer function (**Transfer Fcn**) block shown above implements a transfer function representing a general input output function

$$G(s) = \frac{N(s)}{D(s)}$$

that it is not specific nor restricted to circuit analysis. It can, however be used in modelling and simulation studies.

## Example

Recast Example 7 as a MATLAB problem using the LTI Transfer Function block.

For simplicity use parameters  $R_1 = R_2 = R_3 = 1 \Omega$ , and  $C_1 = C_2 = 1 \text{ F}$ .

Calculate the step response using the LTI functions.

Verify the result with Simulink.

The Matlab solution: [example8.m](#)

## MATLAB Solution

From a previous analysis the transfer function is:

$$G(s) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{-1}{R_1 [(1/R_1 + 1/R_2 + 1/R_3 + sC_1)(sR_3C_2) + 1/R_2]}$$

so substituting the component values we get:

$$G(s) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{-1}{s^2 + 3s + 1}$$

We can find the step response by letting  $v_{\text{in}}(t) = u_0(t)$  so that  $V_{\text{in}}(s) = 1/s$  then

$$V_{\text{out}}(s) = \frac{-1}{s^2 + 3s + 1} \cdot \frac{1}{s}$$

We can solve this by partial fraction expansion and inverse Laplace transform as is done in the text book with the help of Matlab's `residue` function.

Here, however we'll use the LTI block that was introduced in the lecture.

Define the circuit as a transfer function

```
G = tf([-1],[1 3 1])
```

step response is then:


```
step(G)
```

Simple!


## Simulink model

See [example\\_8.slx](#)

```
open example_8
```

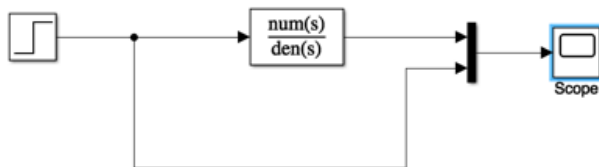

## Result

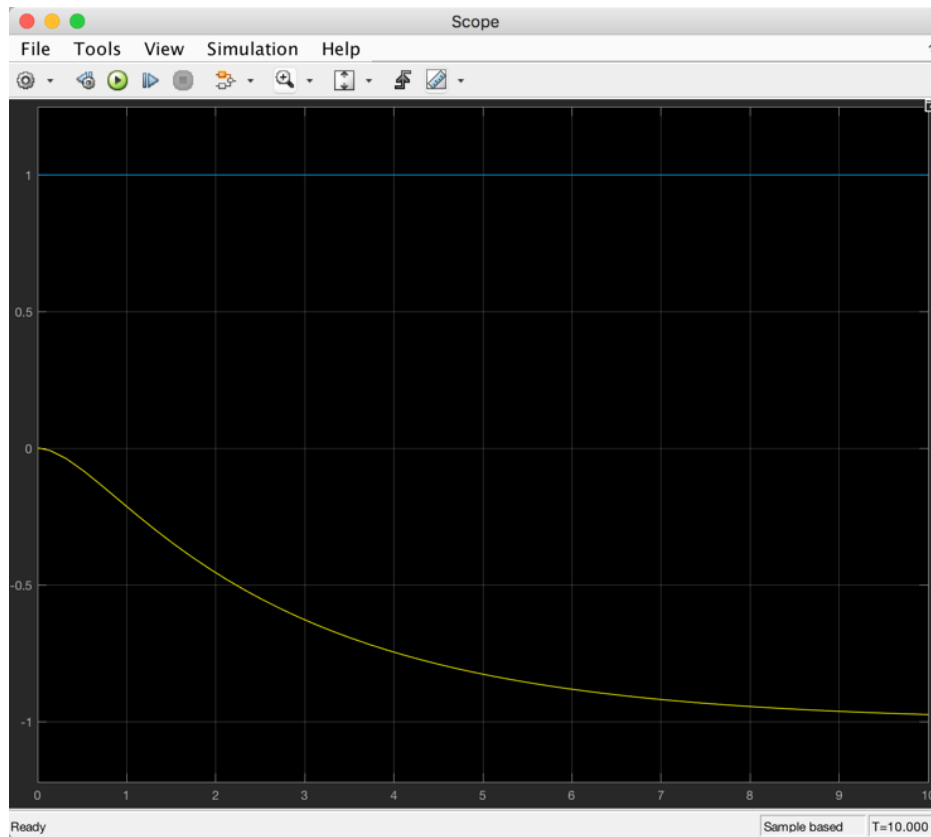

Let's go a bit further by finding the frequency response:

```
bode(G),grid
```

## Matlab Solutions

For convenience, single script MATLAB solutions to the examples are provided and can be downloaded from the accompanying [MATLAB](#) folder.

- Solution 7 [[solution7.m](#)]
- Example 8 [[example8.m](#)]
- Simulink model [[example\\_8.slx](#)]

```
cd ../matlab
ls
open solution7
```



---

By Dr Chris P. Jobling

© Copyright Swansea University (2019-2022).

This page was created by [Dr Chris P. Jobling](#) for [Swansea University](#).