

Homework 3

Using the Laplace Transform for Circuit Analysis

The questions for Homework 3 are all from [Chapter 4 \(https://ebookcentral.proquest.com/lib/swansea-ebooks/reader.action?docID=3384197&ppg=135#ppg=101\)](https://ebookcentral.proquest.com/lib/swansea-ebooks/reader.action?docID=3384197&ppg=135#ppg=101) of Karris{cite} karris .

For copyright reasons, we cannot reproduce the questions here. Instead, please access [section 4.7 \(https://ebookcentral.proquest.com/lib/swansea-ebooks/reader.action?docID=3384197&ppg=135#ppg=121\)](https://ebookcentral.proquest.com/lib/swansea-ebooks/reader.action?docID=3384197&ppg=135#ppg=121) of the online book.

Don't look at the answers until you have attempted the problems.

Circuit analysis

End of Chapter Questions 1 to 4.

Transfer functions

End of Chapter Questions 5 to 8.

Reference

See [Bibliography \(/zbib\)](#).